




Lecture 2

Boolean Arithmetic and ALU

Today u will learn

- Convert truth-table to function and visa versa
- Reducing boolean functions
- Half adder
- Full adder
- Multibit adder
- Multiplexer and demultiplexer
- The Arithmetic Logic Unit (ALU)
- Exercise


Boolean algebra / truth tables

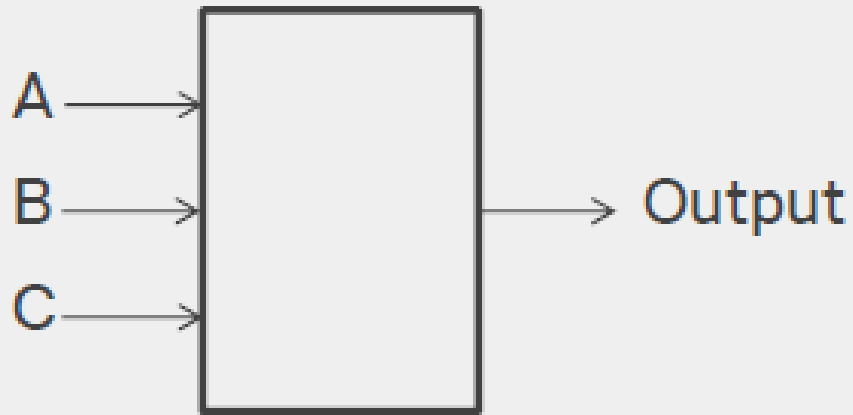


sensor inputs			Output	
A	B	C		
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{A}BC = 1$
1	0	0	0	
1	0	1	1	$A\bar{B}C = 1$
1	1	0	1	$AB\bar{C} = 1$
1	1	1	1	$ABC = 1$

$$\text{Output} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Sum of products

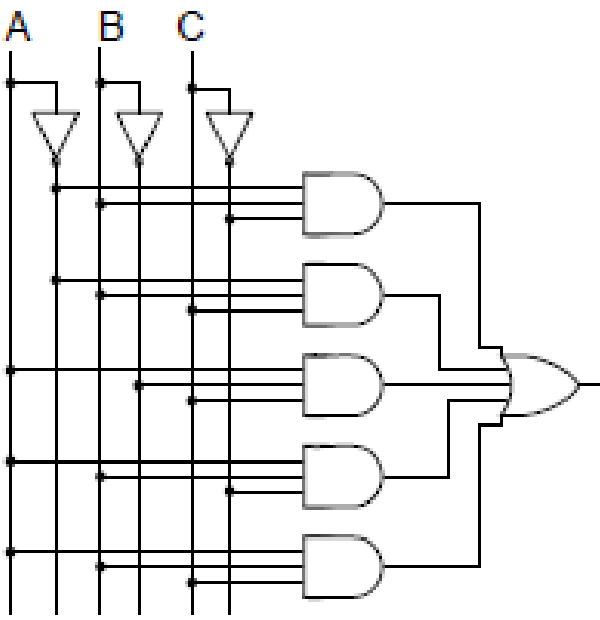Truth Table				Product Terms	Sum-of-Products Expression	Digital Logic Circuit
A	B	C	X			
0	0	0	0		$\overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + A \overline{B} C$	
0	0	1	0			
0	1	0	1	$\overline{A} B \overline{C}$		
0	1	1	1	$\overline{A} B C$		
1	0	0	0			
1	0	1	1	$A \overline{B} C$		
1	1	0	1	$A B \overline{C}$		
1	1	1	1	$A B C$		

KarnaughMaps

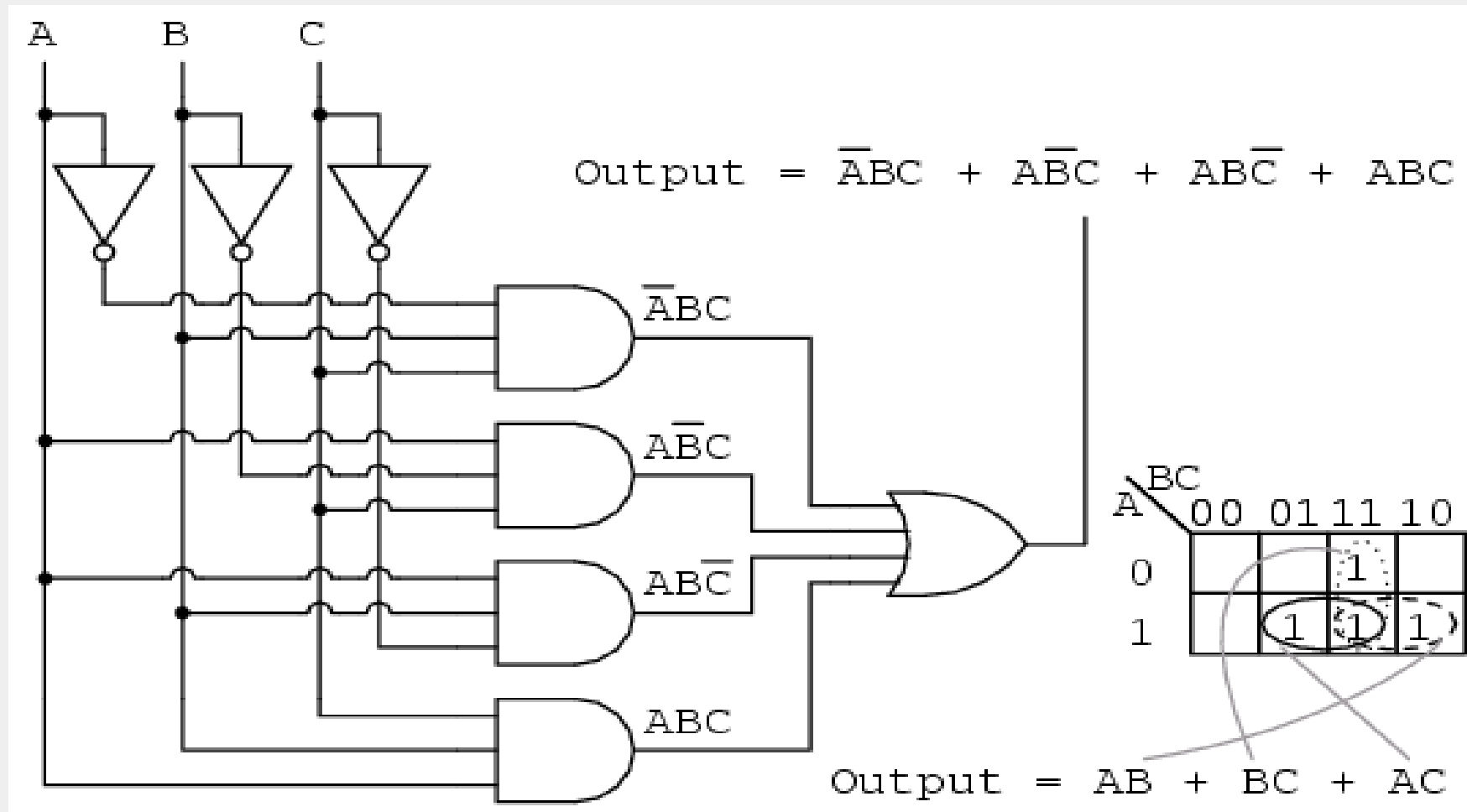

Truth table to Function


- Describe the 1's
- Simplify the expression

$$\overline{A}BC + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

$$\overline{A}C + \overline{A}C + A\overline{B}\overline{C}$$


$$\overline{A}C + A\overline{B}\overline{C}$$

A	B	C	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

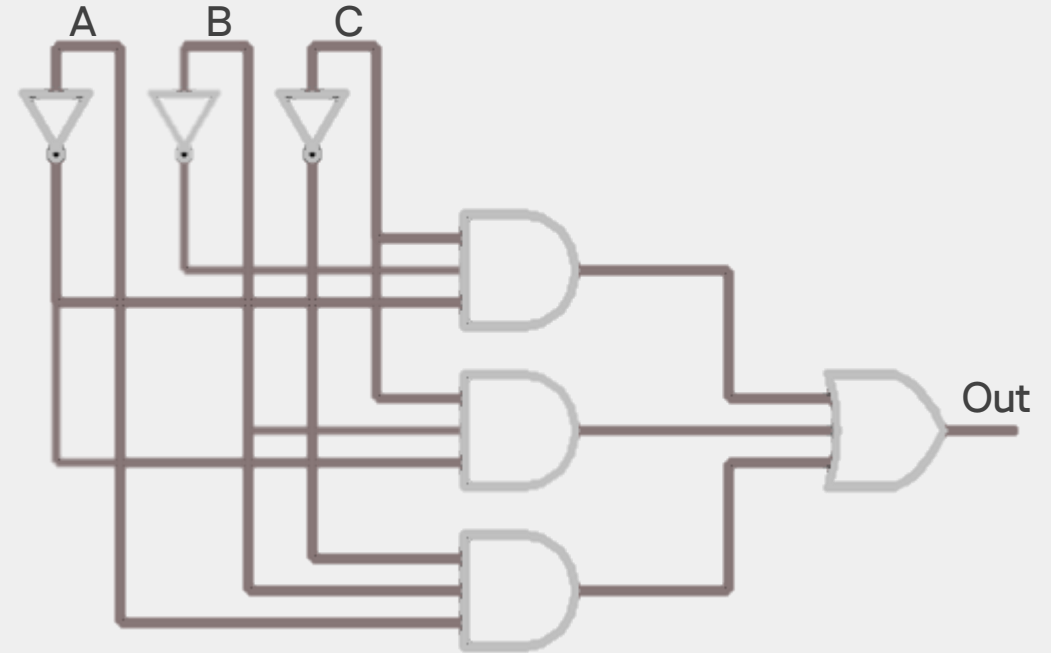

Half- and full-adders

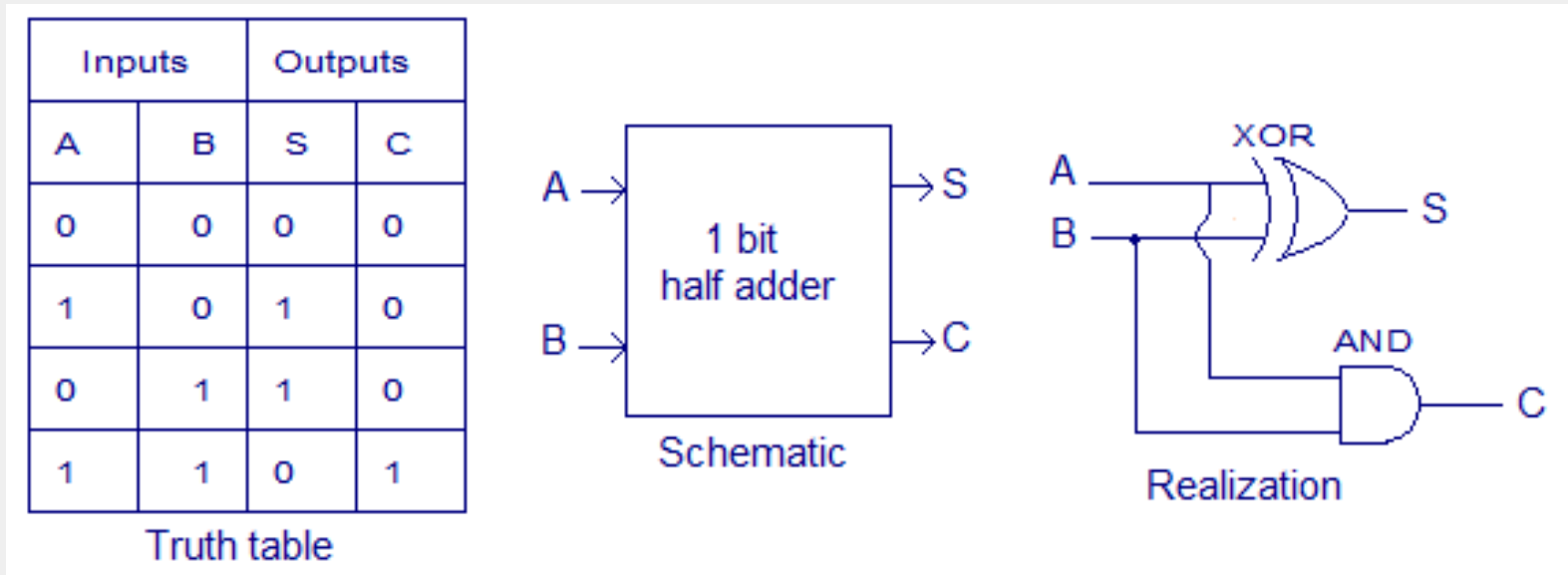
- A half-adder takes two bits and generates sum and carry



<http://tinyurl.com/ybkt6ffj>

Half- and full-adders

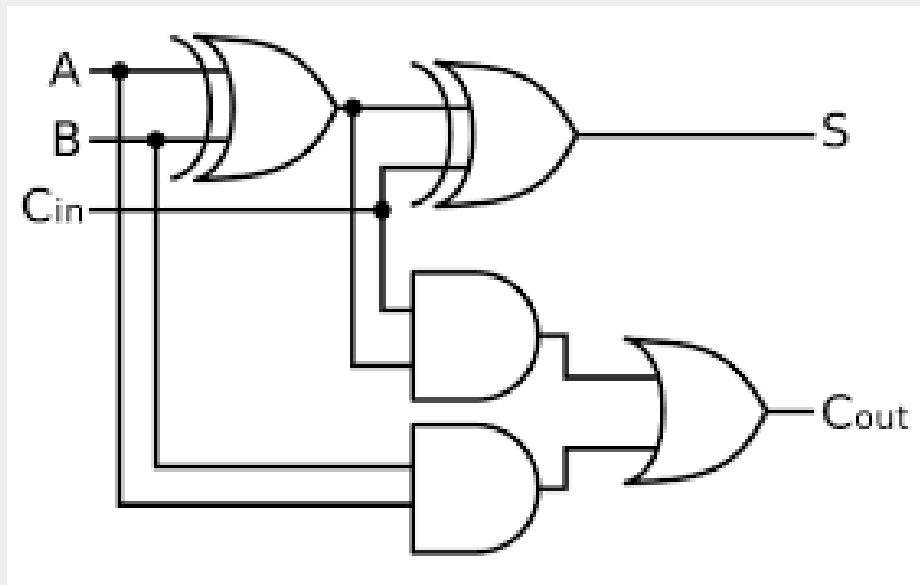
- A full-adder takes two bits and the carry from the previous (lower-order) bit and generates sum and carry:



Input bit for number A	Input bit for number B	Carry bit input C _{IN}	Sum bit output S	Carry bit output C _{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Half- and full-adders

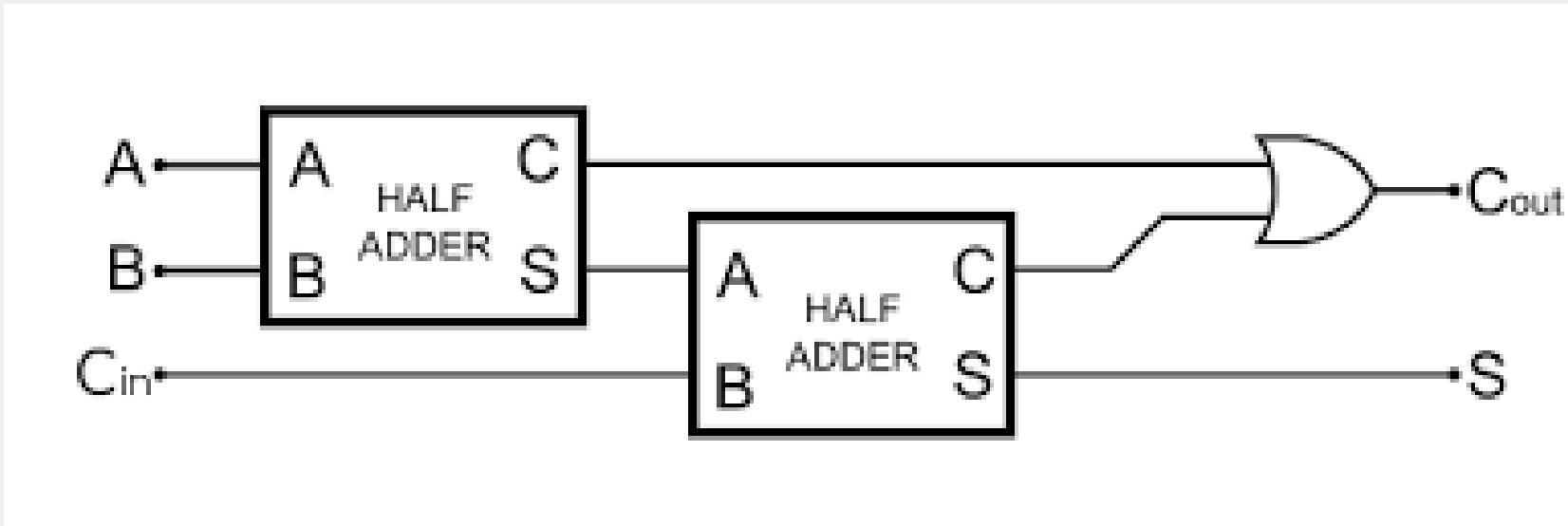- A full-adder can be built using two half adders



Half- and full-adders

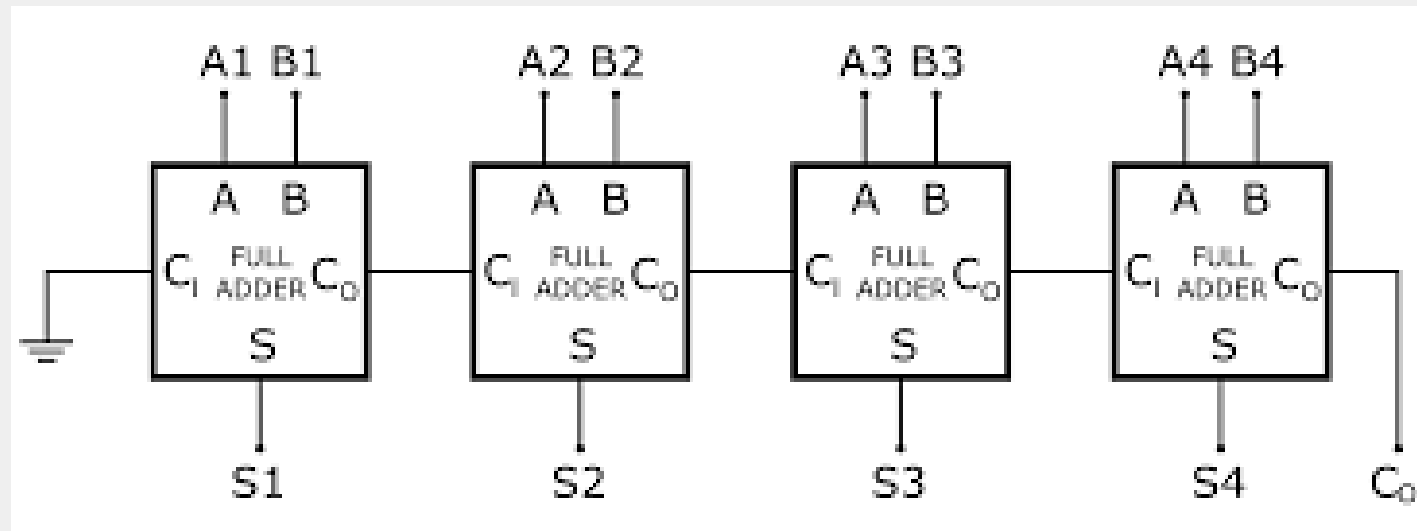- For more info look at link:
http://en.wikibooks.org/wiki/Practical_Electronics/Adders




Multibit adder

- A 4bit adder consist of 4 "Full adder"
- The AVR has an 8 bit adder. The carry from the MSB goes in the status register

Multiplexer


- Used for selecting 1 of multiple inputs
- Has Multiple inputs
- And some select bits

- <http://tinyurl.com/yyc4dz36>

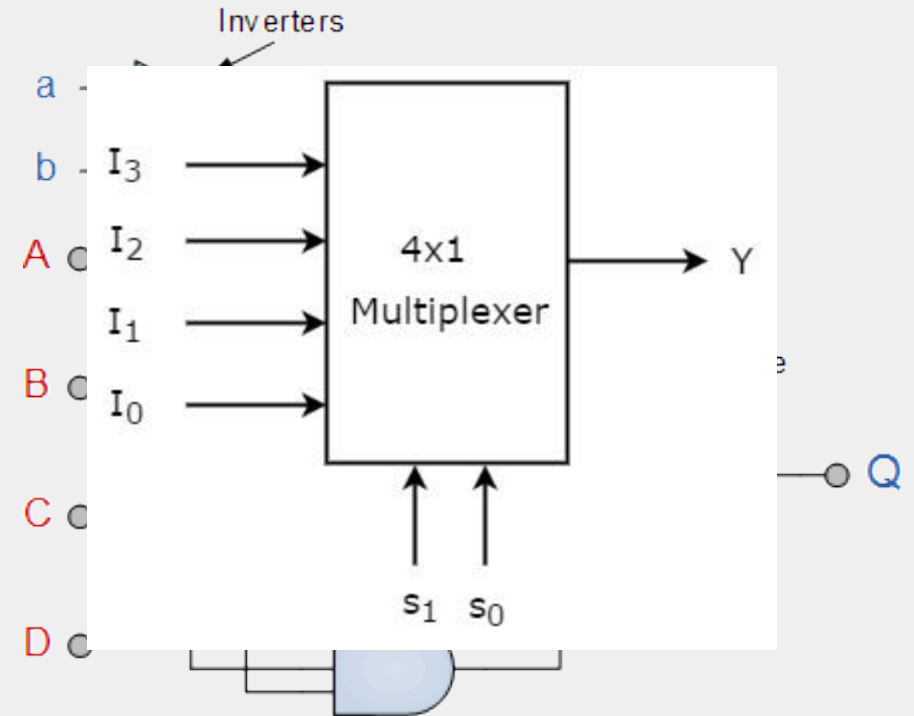

Demultiplexer

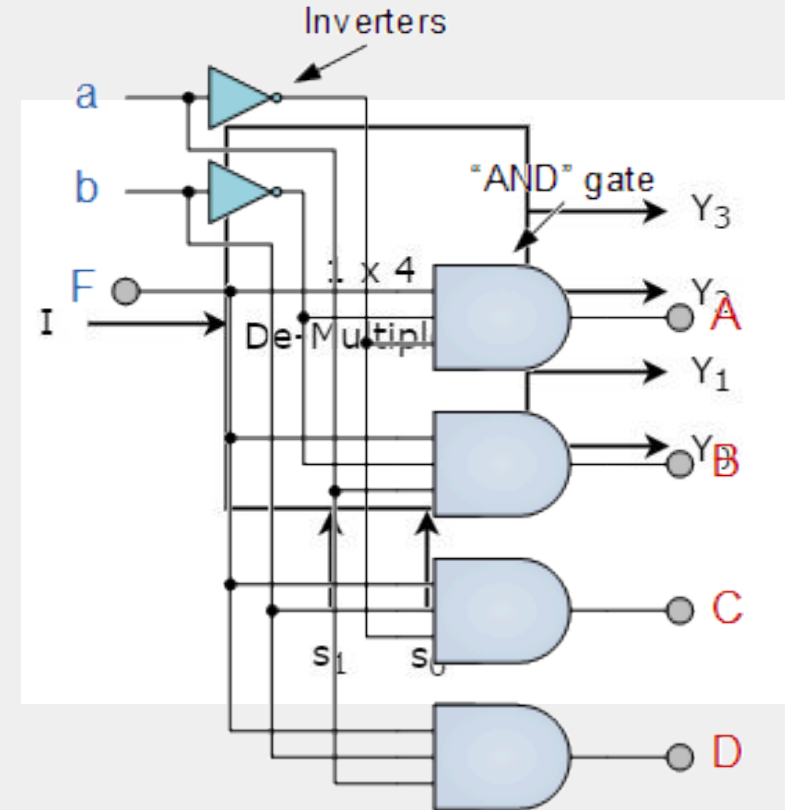- Use to send 1 input to a specific output
- 1 input
- Some select bit




- <http://tinyurl.com/y6cx4qx9>

Computer Architecture Types


–Harvard

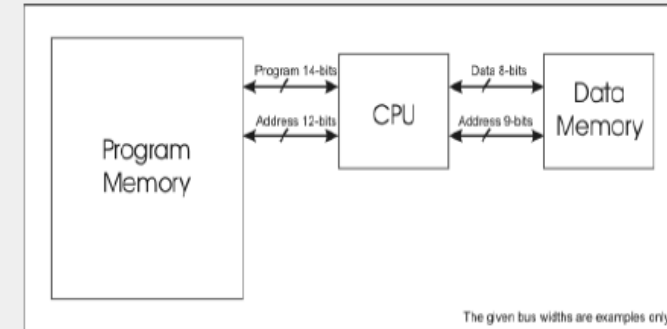- One program bus
- One data bus
- Can work with instructions and data simultaneously




–Von Neumann

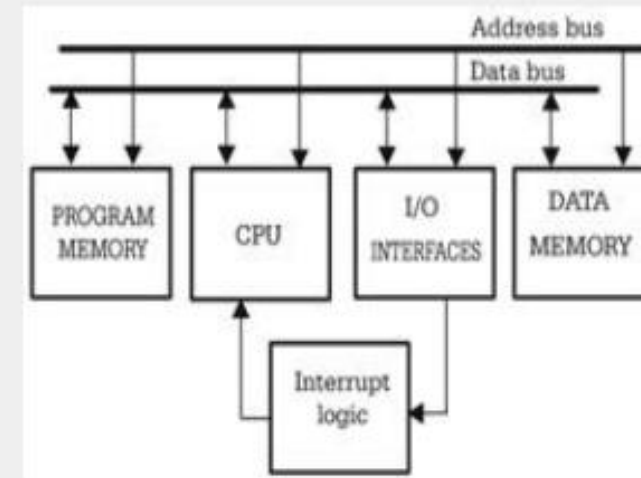- One bus
- Bus holds either instruction or data



Computer organisation

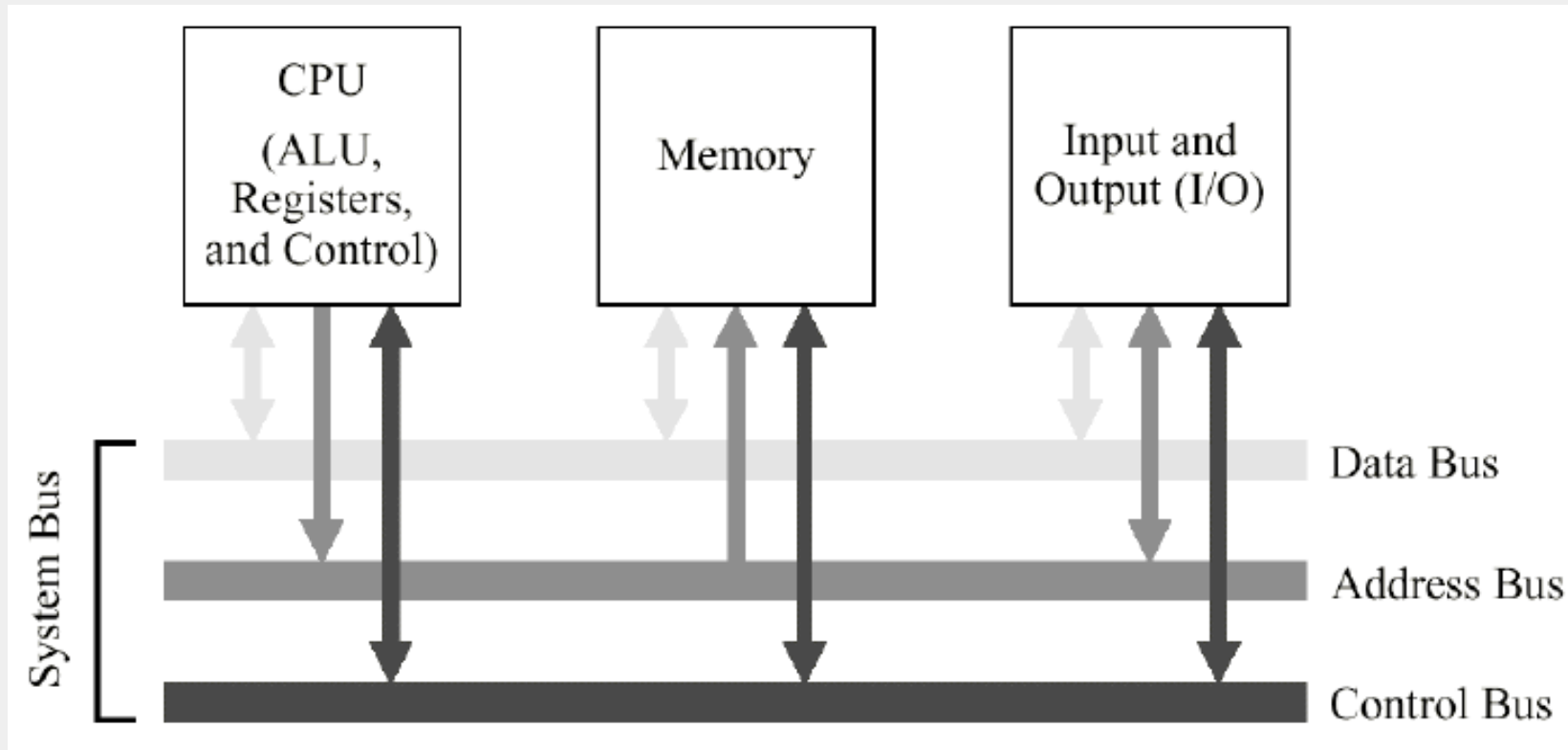

A bus is multiple wires. Could be a 8 wire bus, if the the PC is an 8bit processor



Microprocessor vs. Microcontroller

General purpose computer

- •Highly configurable hw
- •Many applications
- •Different purposes
- •Advanced user interface
- •Human to human communication

Embedded computer

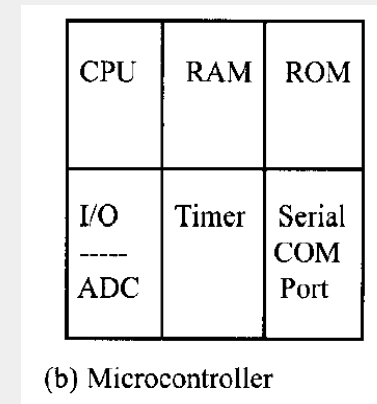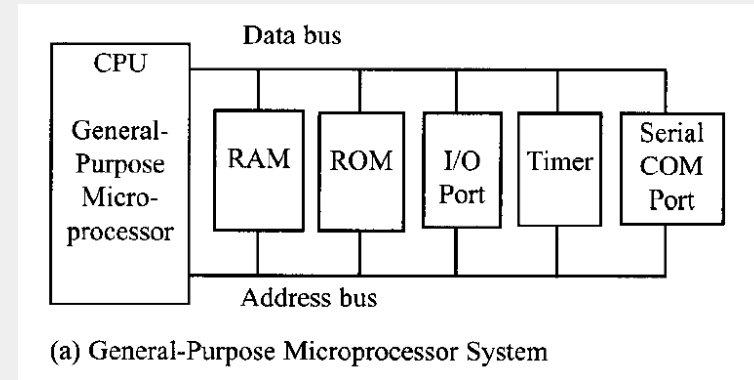
- –Fixed hw configuration
- –Single application
- –One purpose
- –Simple user interface
- –Machine to machine communication



The Central Processing Unit

The CPU typically consists of

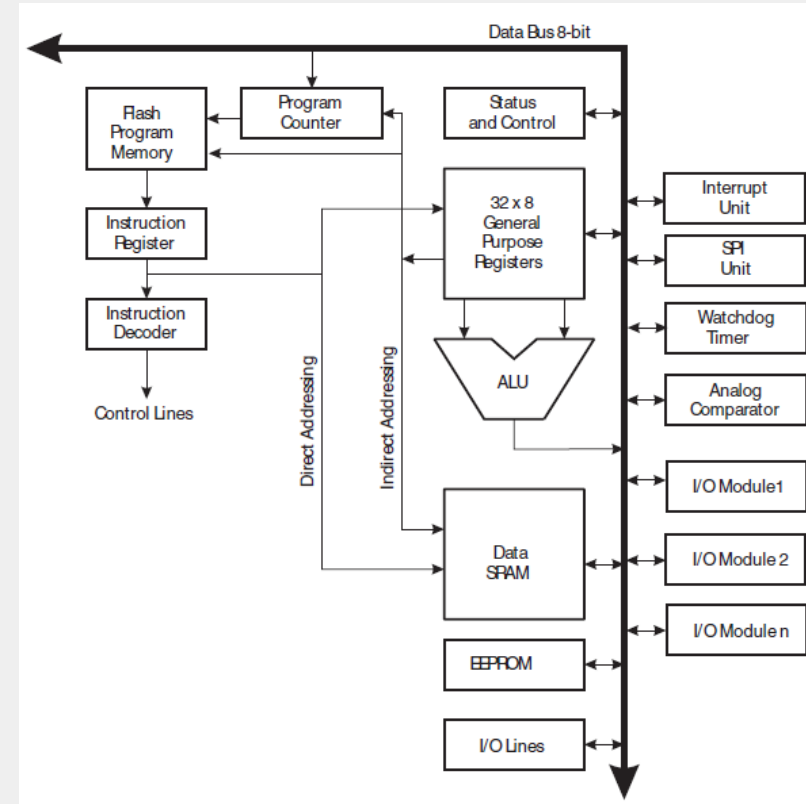- -ALU
- -Program counter
- -Instruction register
- -Instruction decoder
- -Input/Output devices




CPU – Animation

The heart of a computer is the central processing unit or CPU. This device contains all the circuitry that the computer needs to manipulate data and execute instructions.


Some of the circuits of a computer are made of gates
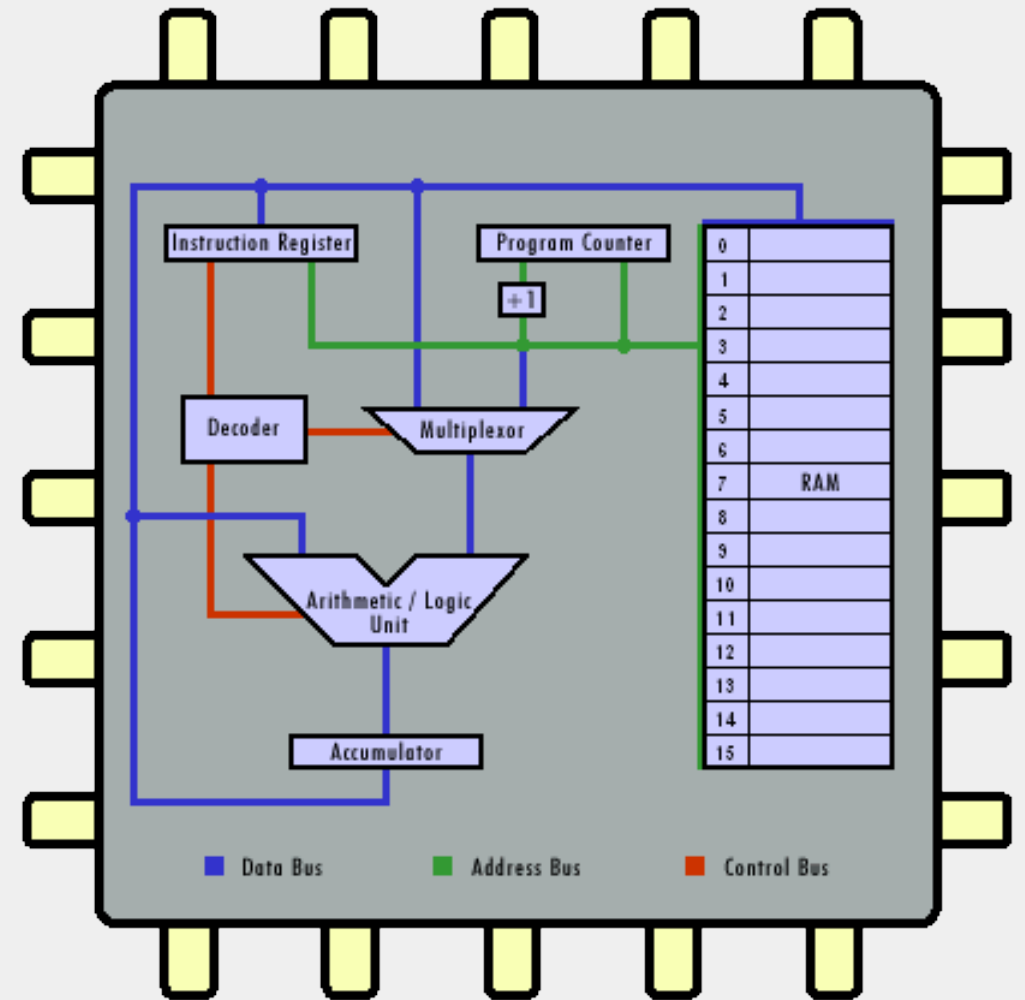
<http://courses.cs.vt.edu/~csonline/MachineArchitecture/Lessons/CPU/Lesson.html>



The Arithmetic Logical Unit (ALU)


- Can do very simple math

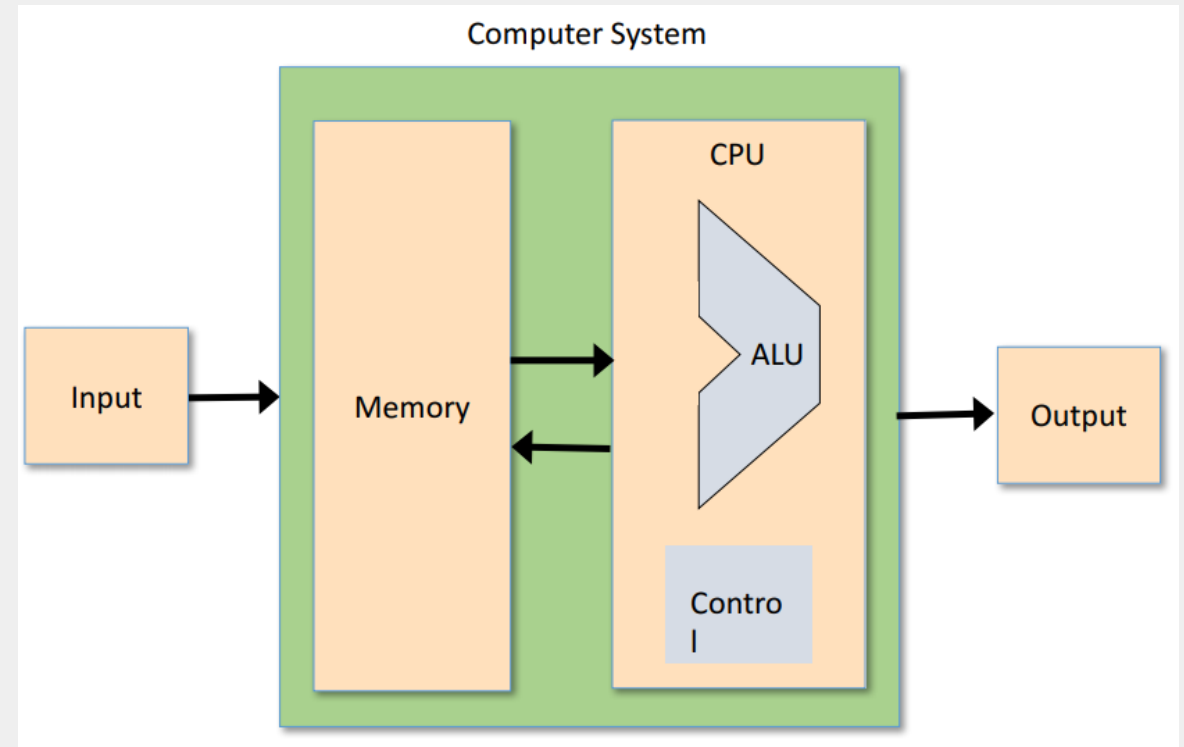

The Arithmetic Logical Unit (ALU)

The Hack ALU

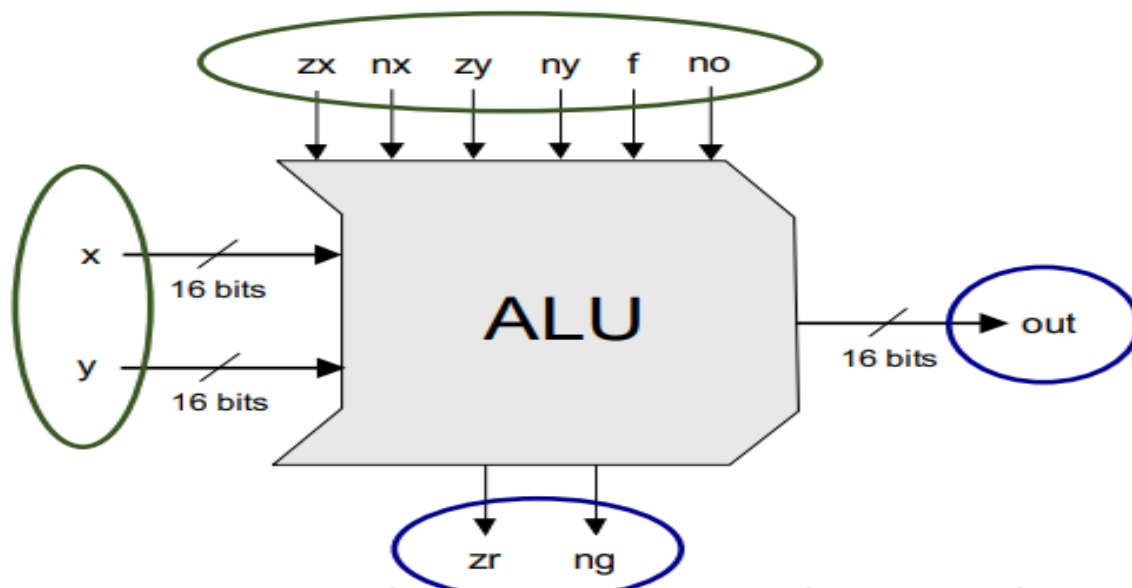- Operates on two 16-bit, two's complement values
- Outputs a 16-bit, two's complement value
- Which function to compute is set by six 1-bit inputs
- Computes one out of a family of 18 functions
- Also outputs two 1-bit values (to be discussed later).




out
0
1
-1
x
y
!x
!y
-x
-y
x+1
y+1
x-1
y-1
x+y
x-y
y-x
x&y
x y

The Arithmetic Logical Unit (ALU)


The Hack ALU

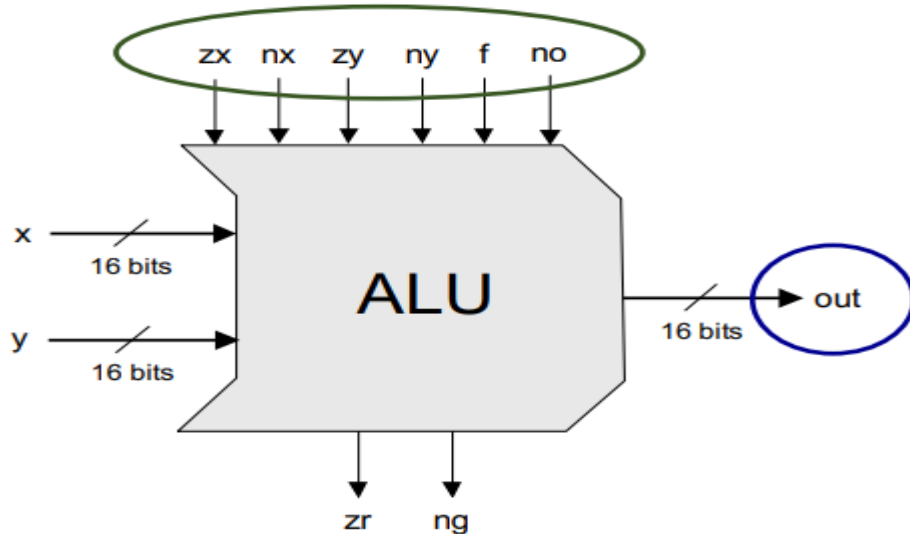To cause the ALU to compute a function, set the control bits to one of the binary combinations listed in the table.



control bits						
zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

The Arithmetic Logical Unit (ALU)

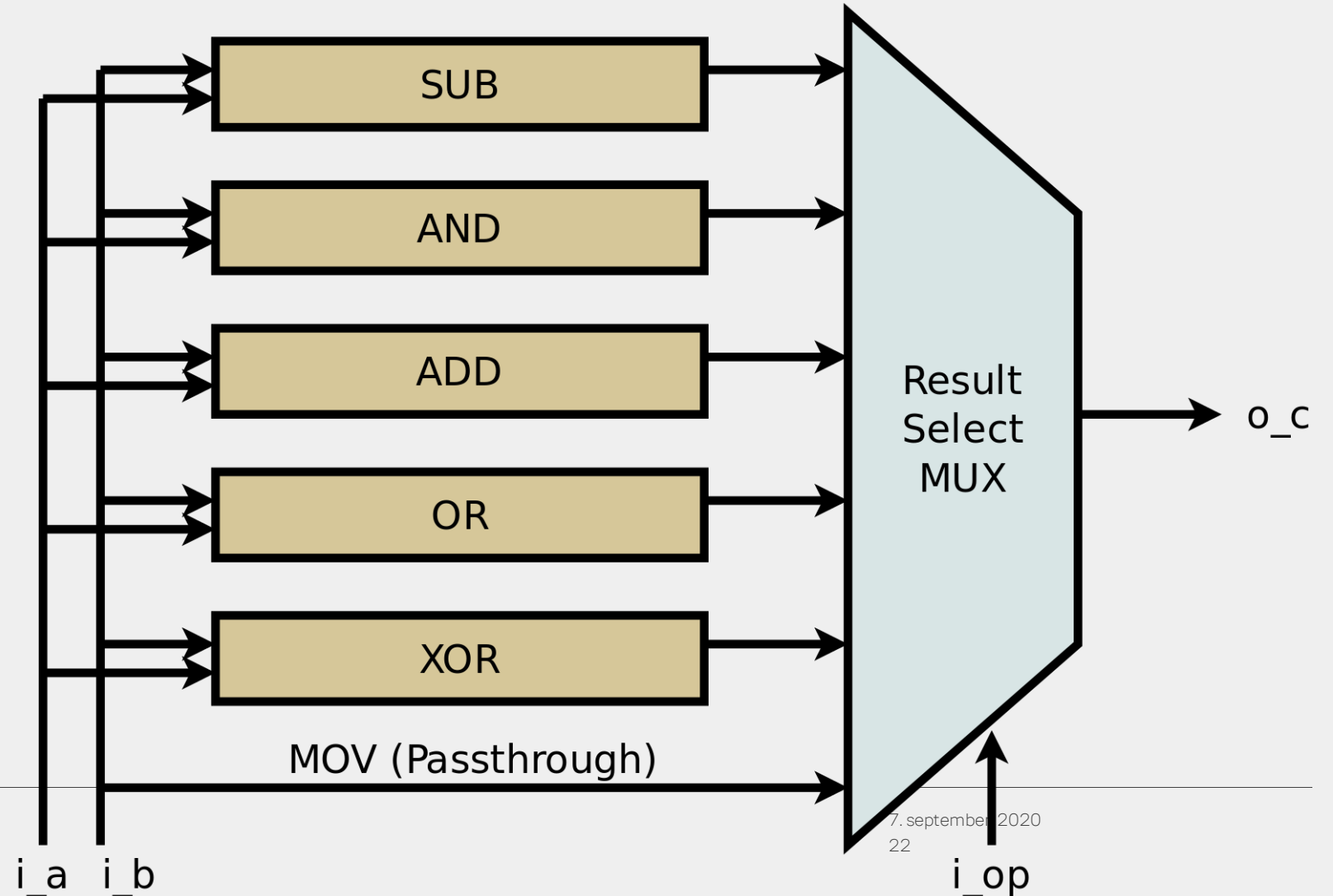

Exercise

- We know how to make OR and XOR from NAND gates. So no reason to do that again.